

RTC Backup Application Note

80000NT10054A Rev.0 - 2011-09-22



Making machines talk.



APPLICABILITY TABLE

PRODUCT
GC864-QUAD V2
GC864-DUAL V2
GE864-QUAD AUTOMOTIVE V2
GE864-QUAD ATEX
GE864-QUAD V2
GE864-GPS
GE865-QUAD
GL865-DUAL
GL868-DUAL





SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE

Notice

While reasonable efforts have been made to assure the accuracy of this document, Telit assumes no liability resulting from any inaccuracies or omissions in this document, or from use of the information obtained herein. The information in this document has been carefully checked and is believed to be entirely reliable. However, no responsibility is assumed for inaccuracies or omissions. Telit reserves the right to make changes to any products described herein and reserves the right to revise this document and to make changes from time to time in content hereof with no obligation to notify any person of revisions or changes. Telit does not assume any liability arising out of the application or use of any product, software, or circuit described herein; neither does it convey license under its patent rights or the rights of others.

It is possible that this publication may contain references to, or information about Telit products (machines and programs), programming, or services that are not announced in your country. Such references or information must not be construed to mean that Telit intends to announce such Telit products, programming, or services in your country.

Copyrights

This instruction manual and the Telit products described in this instruction manual may be, include or describe copyrighted Telit material, such as computer programs stored in semiconductor memories or other media. Laws in the Italy and other countries preserve for Telit and its licensors certain exclusive rights for copyrighted material, including the exclusive right to copy, reproduce in any form, distribute and make derivative works of the copyrighted material. Accordingly, any copyrighted material of Telit and its licensors contained herein or in the Telit products described in this instruction manual may not be copied, reproduced, distributed, merged or modified in any manner without the express written permission of Telit. Furthermore, the purchase of Telit products shall not be deemed to grant either directly or by implication, estoppel, or otherwise, any license under the copyrights, patents or patent applications of Telit, as arises by operation of law in the sale of a product.

Computer Software Copyrights

The Telit and 3rd Party supplied Software (SW) products described in this instruction manual may include copyrighted Telit and other 3rd Party supplied computer programs stored in semiconductor memories or other media. Laws in the Italy and other countries preserve for Telit and other 3rd Party supplied SW certain exclusive rights for copyrighted computer programs, including the exclusive right to copy or reproduce in any form the copyrighted computer program. Accordingly, any copyrighted Telit or other 3rd Party supplied SW computer programs contained in the Telit products described in this instruction manual may not be copied (reverse engineered) or reproduced in any manner without the express written permission of Telit or the 3rd Party SW supplier. Furthermore, the purchase of Telit products shall not be deemed to grant either directly or by implication, estoppel, or otherwise, any license under the copyrights, patents or patent applications of Telit or other 3rd Party supplied SW, except for the normal non-exclusive, royalty free license to use that arises by operation of law in the sale of a product.





Usage and Disclosure Restrictions

License Agreements

The software described in this document is the property of Telit and its licensors. It is furnished by express license agreement only and may be used only in accordance with the terms of such an agreement.

Copyrighted Materials

Software and documentation are copyrighted materials. Making unauthorized copies is prohibited by law. No part of the software or documentation may be reproduced, transmitted, transcribed, stored in a retrieval system, or translated into any language or computer language, in any form or by any means, without prior written permission of Telit

High Risk Materials

Components, units, or third-party products used in the product described herein are NOT fault-tolerant and are NOT designed, manufactured, or intended for use as on-line control equipment in the following hazardous environments requiring fail-safe controls: the operation of Nuclear Facilities, Aircraft Navigation or Aircraft Communication Systems, Air Traffic Control, Life Support, or Weapons Systems (High Risk Activities"). Telit and its supplier(s) specifically disclaim any expressed or implied warranty of fitness for such High Risk Activities.

Trademarks

TELIT and the Stylized T Logo are registered in Trademark Office. All other product or service names are the property of their respective owners.

Copyright © Telit Communications S.p.A. 2011.





Contents

1.	Intr	oduction	6
1.1	۱.	Scope	6
1.2	2.	Audience	6
1.3	3.	Contact Information, Support	6
1.4	, +.	Document Organization	6
1.5	5.	Text Conventions	7
1.6	<i>b</i> .	Related Documents	7
2.	Ove	rview	8
2.1	۱.	Pin out	8
	2.1.1	. GE865	8
	2.1.2	. GL865-QUAD/GL865-DUAL	9
-	2.1.3 ATEX	8. GE864-QUAD/GE864-QUAD-V2/GE864-QUAD AUTOMOTIVE V2/GE864-QUAD K/GE864-GPS/GC864-QUAD/GC864-QUAD-V2	9
2.2	2.	Backup Capacitor	10
	2.2.1	Calculating Backup Capacitor	
	2.2.2	2. Charging the Backup Capacitor	
2.3	3.	Backup Battery	13
3.	Doc	ument History	15





1. Introduction

1.1. Scope

Scope of this document is to give an overview of how to implement in a customer's application a backup battery/capacitor on the Telit modules..

1.2. Audience

This document is intended for customers designing with Telit modules.

1.3. Contact Information, Support

For general contact, technical support, to report documentation errors and to order manuals, contact Telit Technical Support Center (TTSC) at:

TS-EMEA@telit.com TS-NORTHAMERICA@telit.com TS-LATINAMERICA@telit.com TS-APAC@telit.com

Alternatively, use:

http://www.telit.com/en/products/technical-support-center/contact.php

For detailed information about where you can buy the Telit modules or for recommendations on accessories and components visit:

http://www.telit.com

To register for product news and announcements or for product questions contact Telit Technical Support Center (TTSC).

Our aim is to make this guide as helpful as possible. Keep us informed of your comments and suggestions for improvements.

Telit appreciates feedback from the users of our information.

1.4. Document Organization

This document contains the following chapters (sample):

<u>"Chapter 1: "Introduction"</u> provides a scope for this document, target audience, contact and support information, and text conventions.

"Chapter 2: "Overview" gives an overview of the features of the product.





1.5. Text Conventions



<u>Danger – This information MUST be followed or catastrophic equipment failure or bodily</u> <u>injury may occur.</u>



Caution or Warning – Alerts the user to important points about integrating the module, if these points are not followed, the module and end user equipment may fail or malfunction.



Tip or Information – Provides advice and suggestions that may be useful when integrating the module.

All dates are in ISO 8601 format, i.e. YYYY-MM-DD.

1.6. Related Documents

- GE865-QUAD Hardware User Guide, 1vv0300799
- GE/GC864 and GE864-GPS Hardware User Guide, 1vv0300915
- GE864-QUAD Automotive V2 Hardware User Guide, 1vv0300840
- GE864 QUAD ATEX Hardware User Guide, 1vv0300879
- GL865 Hardware User Guide, 1vv0300910
- GL868 DUAL Hardware User Guide, 1vv0300896





2. Overview

This application note describes how to implement in a customer's application a backup battery/capacitor on the Telit modules. The backup battery is necessary if is needed to maintain active the RTC (real time clock) settings if the main power supply of the module (VBATT) is switched off.

2.1. Pin out

The pin for the RTC backup is present on all the products reported below where electrical characteristics are showed.

2.1.1. GE865

The signal is present on the BGA BALL reported on the relative Telit Hardware User Guide.

Parameter	Symbol	Limit V	alues		Unit	Remark
		min.	typ.	max.		
Output Voltage	VRTC	1.86	2.05	2.14	V	
Output current	IRTC	2			mA	VBATT > 3.0 V; VRTC=2.1V
Reverse Current(*)	IRev		10		μΑ	VBATT = 0V
Minimum RTC voltage	VRTC min		1.1		V	

(*)VBATT has to be connected at least one time





2.1.2. GL865-QUAD/GL865-DUAL

The signal is present on the PAD reported on the relative Telit Hardware User Guide.

Parameter	Symbol	Limit V	alues		Unit	Remark
		min.	typ.	max.		
Output Voltage	VRTC	1.86	2.05	2.14	V	
Output current	IRTC	2			mA	VBATT > 3.0 V; VRTC=2.1V
Reverse Current(*)	IRev		20		μΑ	VBATT = 0V
Minimum RTC voltage	VRTC min		1.1		V	

(*)VBATT has to be connected at least one time

2.1.3. GE864-QUAD/GE864-QUAD-V2/GE864-QUAD AUTOMOTIVE V2/GE864-QUAD ATEX/GE864-GPS/GC864-QUAD/GC864-QUAD-V2

The signal is present on the BGA BALL/PIN reported on the relative Telit Hardware User Guide.

Parameter	Symbol	Limit V	alues		Unit	Remark
		min.	typ.	max.		
Output Voltage	VRTC	1.86	2.05	2.14	V	
Output current	IRTC	2			mA	VBATT > 3.0 V; VRTC=2.1V
Reverse Current(*)	IRev		40		μΑ	VBATT = 0V
Minimum RTC voltage	VRTC min		1.1		V	

(*)VBATT has to be connected at least one time





2.2. **Backup Capacitor**

The first solution for the RTC backup is adding a capacitor to the VRTC pin.

2.2.1. **Calculating Backup Capacitor**

In order to define the backup capacitor value for the RTC, knowing the time, we have to consider the following parameters:

- VRTC The Starting voltage of the capacitor (Volt)
- VRTC_{MIN} The minimum voltage acceptable for the RTC circuit. (Volt)
- IRev (Ampere) The current consumption of the RTC circuitry when VBATT = 0
- B_{Time} Backup Time (Hours) .

If we assume that the RTC draws a constant current while running from VRTC (VBATT=0), then calculating the backup capacitor in Farad would use the formula:

$$C = \frac{B_{Time} * IRev}{VRTC - VRTC_{MIN}} * 3600$$

If we have the capacitor value and we want to calculate the Backup Time the formula will be:

$$B_{Time} = \frac{C * (VRTC - VRTC_{MIN})}{IRev * 3600}$$

For example if we have the following data:

- VRTC = 2.05 V
- VRTC_{MIN} = 1.1 V
- $= 10 \, \mu A$ IRev
- B_{Time} = 23 hours

The necessary capacitor will be around 0.9F.





On Figure 1 is reported a simple example of Backup Capacitor connection where capacitor Cooper/Bussmann KR-5R5H105-R is used.

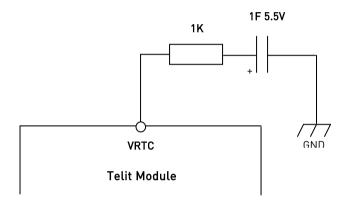


Figure 1



NOTES:

With ON/OFF line connected to GND the IRev will be around 110 μ A. Please consider this for the backup time calculation.

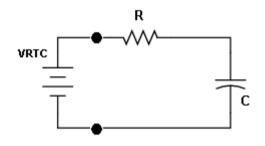




2.2.2. Charging the Backup Capacitor

In order to define the Charging time of the RTC's Backup capacitor we have to consider the following parameters:

- Capacitor Value (e.g. 1 F)
- Capacitor Starting Voltage (e.g. 0V)
- Series Resistor



The time constant of the circuit is R*C. We could consider the capacitor charged after a period of 5T.



WARNING:

In order to guarantee the correct module start-up, the current drawn by VRTC pin don't must exceed 2mA. For this reason, the minimum required series resistor is **1K Ohm**. This guarantee the correct module start-up even if the backup capacitor is completely discharged (voltage on capacitor=0V).

Starting with a 0 volts on capacitor, the voltage drop for the RTC circuit is :

VRTC = 2mA *1K Ohm = 2V.

This voltage allows supplying the RTC part.

When the RTC is supplied only by the capacitor, the voltage drop over the 1K resistor is:

Vr = 1K Ohm * (10 uA) = 10 mV.

This voltage drop is negligible and doesn't affect the circuit functionality.

Considering the above considerations the charging time will be: 5 * 1K Ohm * 1F = 5000 sec (1,38 hours)





2.3. Backup Battery

The second solution for the RTC backup is using a lithium primary battery. The operative voltage for VRTC is lower than the voltage of primary lithium battery (3V nominal). It is necessary to put a LDO voltage regulator in the circuit. The suggested circuit is reported on Figure 2.

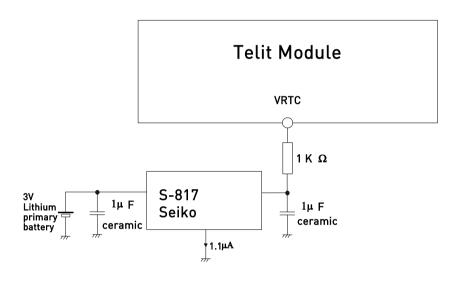


Figure 2

The S-817 Seiko Instruments Inc. LDO has a typical quiescent current value of 1.1μ A. When VBATT is not applied the VRTC Reverse Current (IRev) is 10 uA (see Paragraph 2.1.1). Considering a typical capacity of 220 mAh for a Lithium Primary we can calculate briefly the life time of the battery when VBATT is not applied.

 $\frac{220000 \ \mu Ah}{(1.1+10)\mu A} = 19820 \ hours \rightarrow more \ than \ 2 \ years$

When VBATT voltage is present, the VRTC voltage exceeds the S-817 output voltage, so the current for the Lithium Primary Battery is typically 1.1 μ A and the Lithium Primary Battery duration will be increased.







NOTES:

With ON/OFF line connected to GND the IRev will be around 110 μ A. Please consider this for the backup time calculation.



WARNING:

In this configuration VBATT has to be applied at least one time to setup the RTC circuit of the modem.





3. Document History

Revision	Date	Changes
ISSUE#0	2011-08-09	First ISSUE

